

Power Factor


The Cosine of angle between Voltage and Current in A.C System is called power factor.

For Inductive Circuit Current lags the

Voltage by angle ϕ then power factor is known as lagging Power factor

In Capacitive Circuit Current leads the

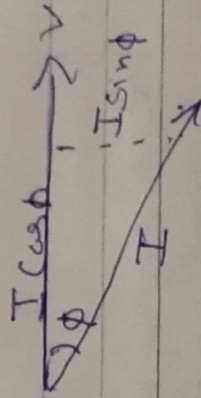Voltage then power factor is known as leading power factor



Phasor diagram of Inductive Circuit

V is taken as reference vector, and I lags V by angle ϕ in case of Inductive Circuit.

The Horizontal Component of Current is


known as $I \cos \phi$ (known as Active Component of Current) which is in phase with Voltage

whereas Vertical Component of Current $I \sin \phi$

is known as Reactive Component of Current

If all the three sides are multiplied by

Voltage V power triangle is obtained

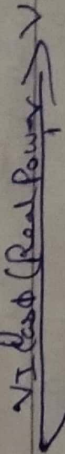

- $VI \cos \phi$ Real power in kW
- $VI \sin \phi$ Reactive power in kVAR
- VI Apparent power in kVA

Power factor = $\frac{\text{Real Power}}{\text{Apparent power}} = \frac{VI \cos \phi}{VI}$

Disadvantage of low power factor

Power consumed in single phase A.C

Circuit $P = VI \cos \phi$
 $I = \frac{P}{V \cos \phi}$

In case of 3 phase A.C

$P = \sqrt{3} VI \cos \phi$
 $I_L = \frac{P}{\sqrt{3} V_L \cos \phi}$

Here load current is inversely proportional to power factor, for fixed power & Voltage.
Lower power factor, higher the current & vice versa

- (1) Greater conductor size: To transmit fixed amount of power at fixed voltage at lower power factor. The conductor will have to carry amount of current which required large conductor size

2 Large Copper losses - Due to more current carried by conductors I²R losses will increase which result to poor efficiency in transmission.

3 Poor Voltage Regulation - Due to low P.F and increased current the voltage in transformer alternator & transmission line.

4 Large KVA rating of equipment
Output power of Alternator & transformer core rated in Apparent Power KVA

$$KVA = \frac{KW}{\cos \phi}$$


Rating is inversely proportional to Power factor. At lower power factor KVA will increase. At low P.F equipment of high KVA is required which is large in size & costly.

CAUSES OF low P.F

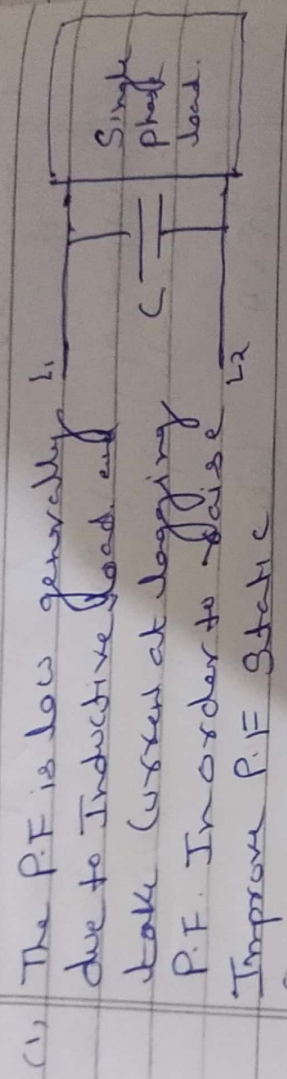- (1) Transformers are inductive devices which causes current to lag behind voltage. At normal load, magnetizing current does not effect too much but at low load, magnetizing current effect too much & lower P.F.


2 In Industry heavy Induction motor run on inductive load which have low P.F. Normally P.F 0.8 to 0.85 ~~low~~ when operating at full load & 0.3 to 0.5 when running at light load.


Power factor Improvement. Using Static Capacitor.



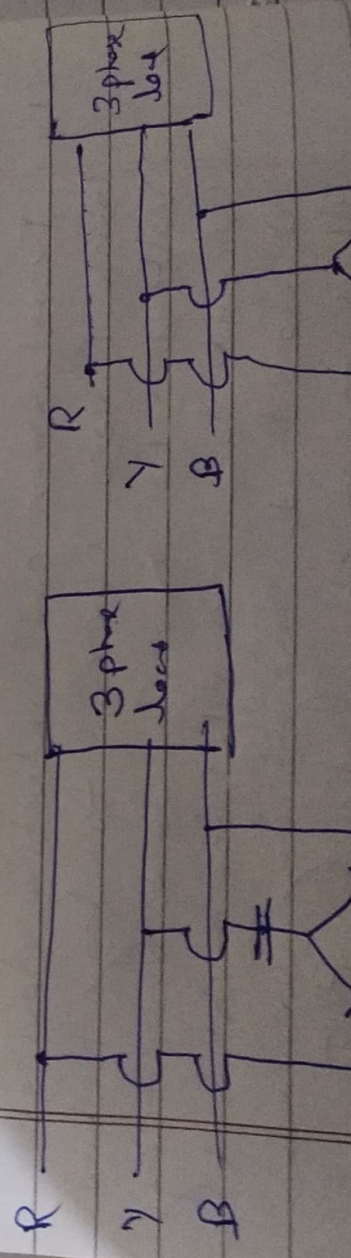(1) The P.F is low generally due to Inductive load. It take current at lagging P.F. In order to raise P.F. Improve P.F. Static Capacitor is connected in parallel with load. The static capacitor draws a current which leads voltage & neutralises the lagging component.

For 3 phase load. Capacitor are connected in Star or delta



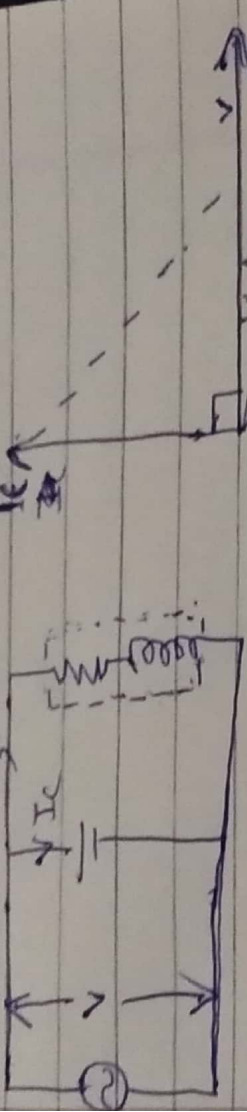

As Capacitor C is connected in parallel with load. The Capacitor current I_C leads voltage by 90° . The resultant current I_1 is vector sum of I & I_C and its angle of lag is now ϕ_2 which is less than ϕ_1 . The value of $\cos \phi_2$ is more than $\cos \phi_1$. Hence P.F. of load is improved from $\cos \phi_1$ to $\cos \phi_2$.