

Hands out on Feedback in amplifier

A- Basic principles and types of feedback

⇒ Feedback is the process by which a fraction or part of output energy of an amplifier is injected back to combine with its input as shown in the diagram:

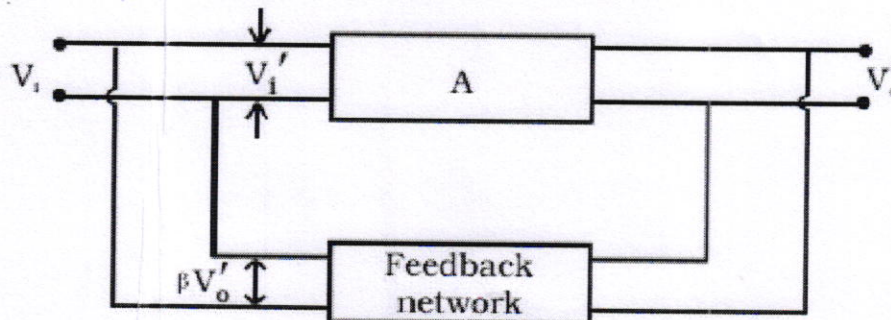


Fig. Feedback amplifier

⇒ The output injected back may aid or oppose the input signal & on this basis feedback can be of two types:

1. **Positive or regenerative feedback**
2. **Negative or degenerative feedback**

1- Positive or regenerative feedback : When the fraction of output injected back is in phase with the input signal & aids with it, it is called **positive or regenerative** feedback.

Adv: Overall gain of amplifier is increased.

Disadvantage: 1- Increased Noise & distortion in output.

2- Results in poor stability

Application: In Oscillator circuits .

2. Negative or degenerative feedback : In case the fraction of output injected back is in opposition or 180° out of phase with input signal, it is known as negative or degenerative feedback.

Adv: 1- Decreased Noise & distortion in output.

2- Improved stability

Disadvantage: 1- Overall gain of amplifier is decreased.

Application: widely used in amplifier circuits .

⇒ **Types Of Feedback on the basis of Electrical Quantity:**

On this Basis the feedback can be classified as below:

1- Voltage Feedback

2- Current feedback

⇒ Both voltage or current can be fed back to input either in series or in shunt.

⇒ Where series feedback connections generally increase input impedance, the shunt feedback connections tend to decrease input impedance.

⇒ On other hand voltage feedback decreases output impedance whereas current feedback decreases output impedance.

B- Derivation of expression for gain of an amplifier employing feedback:

⇒ Let V_1 be input to amplifier & V_o be output of the amplifier Without feedback. In This Condition Voltage Gain A_v Of this amplifier will be given as

$$A_v = V_o / V_1$$

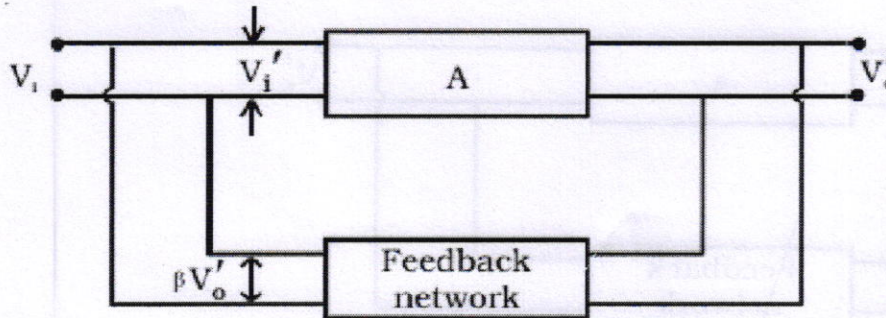


Fig Feedback amplifier

Calculation of gain with feedback

⇒ When a feedback network is employed than the new input to the amplifier is

$$V_1' = V_1 \pm \beta V_o$$

($V_1' = V_1 + \beta V_o$ for Positive Feedback & $V_1' = V_1 - \beta V_o$ For negative feedback)

Where β is factor of feedback circuit, the value of which depends on the type of feedback network used.

⇒ Value of $\beta < 1$ when the feedback network consists of passive components only & $\beta > 1$ if there are active components in the feedback network .

⇒ Let us consider calculation of gain for a negative feedback amplifier. For such an amplifier, new input value will be

$$V_1' = V_1 - \beta V_o$$

⇒ Now Gain of this amplifier will be $A_v = V_o / V_1' = V_o / (V_1 - \beta V_o)$

$$\text{or alternatively } A_v \times (V_1 - \beta V_o) = V_o$$

$$\text{or } A_v \times V_1 - A_v \times \beta V_o = V_o$$

$$\text{or } A_v \times V_1 = (V_o + A_v \times \beta V_o) = V_o (1 + \beta A_v)$$

$$\text{or } A_v / (1 + \beta A_v) = V_o / V_1 = A_v'$$

Where A_v' is the gain of amplifier with negative feedback

Similarly gain for an amplifier with positive feedback can be calculated & that comes out to be

$$A_v' = A_v / (1 - \beta A_v)$$

⇒ The expression for gain with feedback shows that the gain is affected after using feedback circuit.

C- Effect of Negative feedback on gain stability, distortion and bandwidth of an amplifier

1- Increased Gain stability :

⇒ Gain of an amplifier may change due to change either in power supply or in parameters of active device used. Change in gain adversely affects overall performance of an amplifier & therefore needs stability.

⇒ Using negative feedback makes gain stable & thus results in better performance of the amplifier .

⇒ As we know, gain of an amplifier with negative feedback is given as

$$A_v' = A_v / (1 + \beta A_v)$$

⇒ If by any means we are able to make $\beta A_v \gg 1$, then quantity 1 in expression $(1 + \beta A_v)$ can be neglected & in that condition

$$1 + \beta A_v = \beta A_v$$

⇒ In this condition above expression (i) will be read as


$$A_v' = A_v / \beta A_v = A_v' = 1 / \beta$$

⇒ Thus we see that that by just making $\beta A_v \gg 1$, the overall gain of negative feedback amplifier becomes independent of internal gain & depends inversely on feedback factor β .

⇒ This Shows that using negative feedback increases gain stability & thus overall performance of amplifier is improved.

2- Reduction in Distortion & noise:

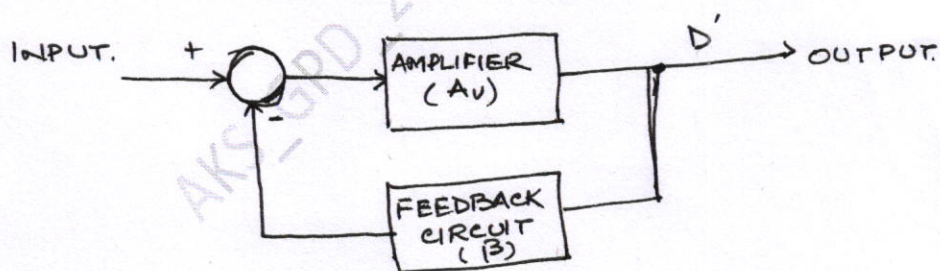⇒ When negative feedback is employed in an amplifier, the harmonic distortion is reduced, this can be understood by the following block diagram:



⇒ Let us assume that the amplifier with gain A_v produces distortion D . When feedback is applied the gain becomes A_v' & the distortion D' .

⇒ The distortion changes as a part of distortion D' is fed to input through the feedback network & this amounts to be $\beta D'$ as shown in above diagram.

⇒ This distortion $\beta D'$ is amplified by gain A_v of the amplifier & due to negative feedback D' is expressed as

$$D' = D - \beta A_v D'$$

$$\text{or } D' = D / (1 + \beta A_v)$$

⇒ Thus we see that in an amplifier with feedback, distortion is reduced by a factor of $(1 + \beta A_v)$

⇒ Similarly it can be shown that in an amplifier with negative feedback, noise level in output is reduced in the same magnitude.

3- Effect of Negative feedback on Frequency response & Bandwidth:

⇒ As we know, overall gain of an amplifier with negative feedback decreases & is given by the following expression:

$$A_v' = A_v / (1 + \beta A_v) \text{ Where } A_v \text{ is gain of amplifier}$$

⇒ With change in gain by a factor of $(1 + \beta A_v)$, the upper & lower cut off frequency are also affected by this factor.

⇒ In fact the lower cut off frequency is decreased & upper cut off frequency is increased by a factor of $(1 + \beta A_v)$, when negative feedback is employed in an amplifier circuit.

⇒ This causes an increase in bandwidth (BW) because BW is difference of upper & lower cut off frequencies.

⇒ Thus, it is concluded that with negative feedback in amplifier, the bandwidth increases & the frequency response is improved.

4- Effect of Negative feedback on Input Impedance :

⇒ It is found that input impedance of an amplifier after employing negative feedback is given as :

$$Z_i' = Z_i (1 + \beta A_v) \text{ Where } Z_i' = \text{Input Impedance after negative feedback}$$

Z_i = Input Impedance without feedback

β = Feedback factor of feedback network

A_v = Gain of amplifier without feedback.

⇒ The above expression clearly shows that input impedance is increased by factor of $(1 + \beta A_v)$ after negative feedback is applied.

4- Effect of Negative feedback on output Impedance :

⇒ It is found that output impedance of an amplifier after employing negative feedback is given as :

$$Z_o' = Z_o / (1 + \beta A_v) \text{ Where } Z_o' = \text{Output Impedance after negative feedback}$$

Z_o = output Impedance without feedback

β = Feedback factor of feedback network


A_v = Gain of amplifier without feedback.

⇒ The above expression clearly shows that output impedance is decreased by factor of $1/(1 + \beta A_v)$ after negative feedback is applied.

D-CONCEPT OF FEEDBACK CIRCUIT


⇒ A feedback circuit is essentially a voltage divider circuit whose primary function is to feed a fraction of output voltage back to input of the amplifier circuit.

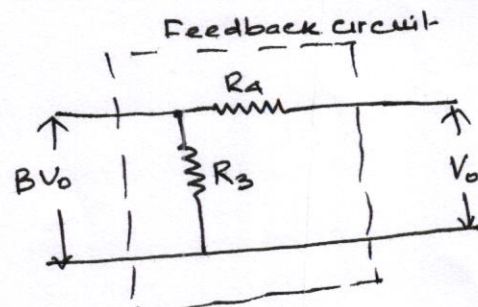⇒ The block of feedback circuit contains two resistors R_3 & R_4 as shown in the adjacent circuit diagram .



E- RC coupled amplifier with emitter bypass capacitor :

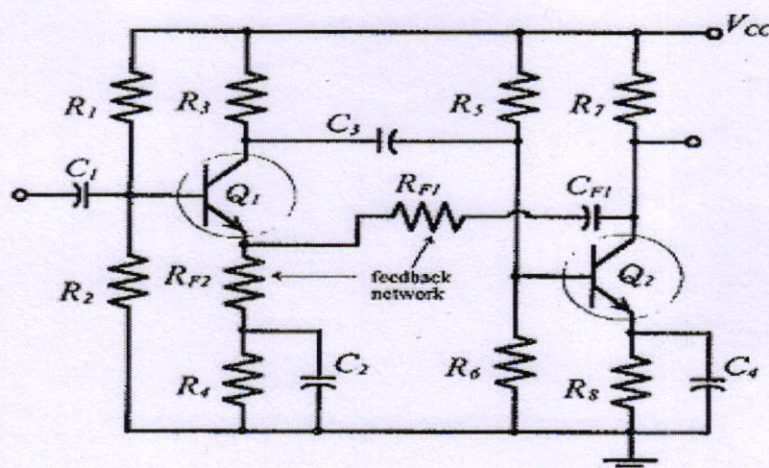⇒ Also Known as two stage Common emitter amplifier with series negative feedback where a two stage RC coupled amplifier is facilitated with suitable arrangement to provide negative feedback as shown in the diagram:



⇒ The additional components R_1 , R_2 & C_1 incorporated in usual two stage RC Coupled amplifier constitute the feedback network.

⇒ The Output voltage is divided across the resistors R_1 , R_2 to produce feedback voltage that is in series with signal at base of transistor Q_2 .


⇒ The capacitor C_1 behaves as open circuit to DC & as short circuit to AC & thus used as dc blocking capacitor to prevent the DC voltage at collector of transistor Q_2 from affecting bias condition of transistor Q_1 .

F -Emitter follower amplifier and its application

⇒ Also known as common collector amplifier circuit, it is a very useful negative current feedback circuit ideal for impedance matching.

⇒ The most important characteristic of this circuit is it's high input impedance & low output impedance.

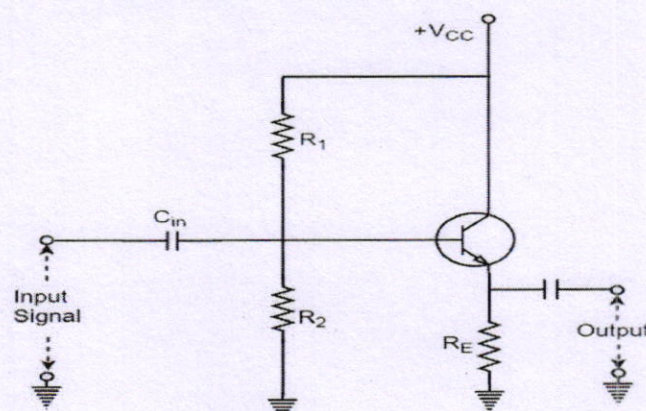⇒ Typical circuit of an emitter follower is shown below:



⇒ When input is applied, resulting current i_e flows through R_E & produces output voltage V_o across R_E means $V_o = i_e R_E$. This voltage V_o opposes the signal voltage & thus provides negative feedback.

⇒ Moreover the voltage V_o fed back to input is proportional to emitter current, that's why the circuit is called a negative current feedback circuit.

⇒ Since in this configuration, output voltage which is in fact emitter voltage, follows the input voltage, hence this circuit is known as emitter follower.


⇒ Gain of this amplifier is less than 1

⇒ Input impedance of this amplifier is given as $\beta R_E + R_i$

⇒ Output impedance is very Low & is given by $R_o / (1 + \beta)$

G- Darlington Amplifier

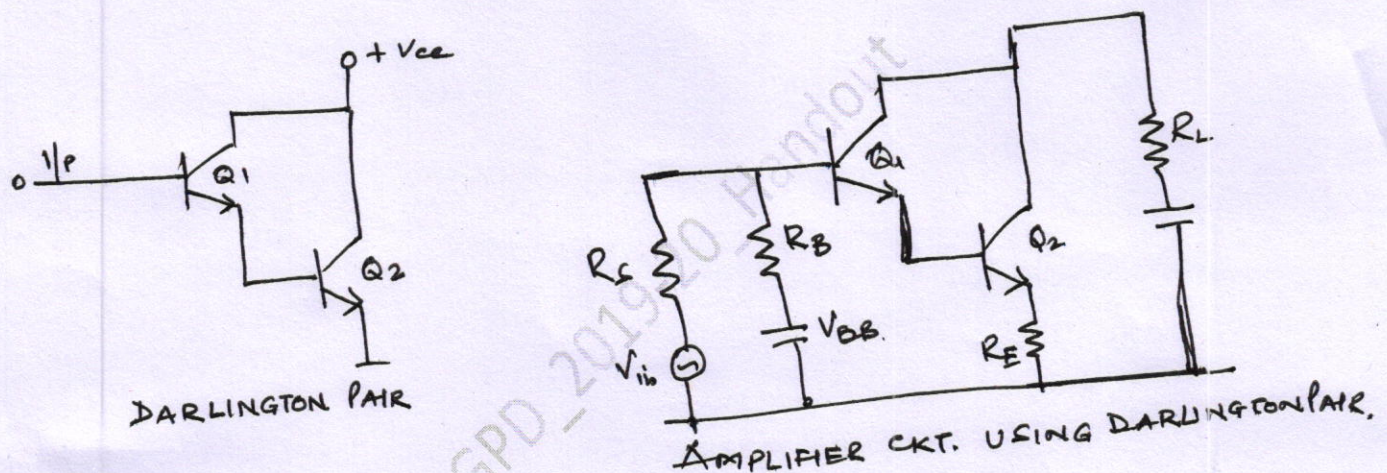⇒ Here an interconnection of two bipolar junction transistors as a single unit is used. Normally one BJT is low power while the other one has high power. this unit is commercially known as Darlington pair after its inventor. Darlington pair & amplifier circuit using such pair is shown below:



⇒ The Emitter of one transistor is connected to the Base of the other to produce a more sensitive transistor with a much larger current gain being useful in applications where current amplification or switching is required.

⇒ Main feature of this amplifier circuit is that the two BJT work as a single transistor with its current amplification ratio as the product of current amplification ratios of the individual BJT. In other words, if β_1 & β_2 are current amplification ratio of the two BJT then overall amplification factor β of Darlington pair is given as $\beta = \beta_1 \times \beta_2$

⇒ Such amplifiers are used where high gain is required at a low frequency like Power regulators, Audio **amplifier** output stages.